

# 1 Experiment No. 2

## 2 Experiment Title

## 3 Objective

The objectives of this lab are as follows:

- content...

## 4 Theory

## 5 Required Apparatus

## 6 Circuit Diagram

## 7 Data Table

No of Obs.	Voltmeter Reading in Volts (V)	Ammeter Reading in Ampere (A)	Wattmeter Reading in Watt (W)	Resistance $R = \frac{W}{I^2}$ ( $\Omega$ )	Impedance $Z = \frac{V}{I}$ ( $\Omega$ )	Reactance $X_L = \sqrt{Z^2 - R^2}$ ( $\Omega$ )	Inductance $L = \frac{X}{2\pi f}$ (H)
1.	100	0.2	2	50	502	499.5	1.589
2.	150	0.45	4.4	21.72	333.33	332.6	1.058
3.	200	0.625	7	17.92	526.31	319.49	1.017

## 8 Calculations

The following calculations were performed for each observation to determine the electrical parameters: Resistance ( $R$ ), Impedance ( $Z$ ), Reactance ( $X_L$ ), and Inductance ( $L$ ). The frequency of the circuit was maintained at  $f = 50$  Hz.

1. For  $V = 100$  V ,  $I = 0.2$  A,  $W = 2$  W and  $f = 50$  Hz

(a)

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{500^2 - 50^2} = \sqrt{250000 - 2500} = \sqrt{247500} \approx 497.5 \Omega$$

(b)

$$L = \frac{X_L}{2\pi f} = \frac{497.5 \Omega}{2\pi \times 50 \text{ Hz}} \approx \frac{497.5}{314.16} \approx 1.585 \text{ H}$$

2. for  $V = 150$  V ,  $I = 0.45$  A  $W = 4.4$  W and  $f = 50$  Hz

(a)

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{333.33^2 - 21.72^2} \approx \sqrt{110639.33} \approx 332.6 \Omega$$

(b)

$$L = \frac{X_L}{2\pi f} = \frac{332.6 \Omega}{2\pi \times 50 \text{ Hz}} \approx \frac{332.6}{314.16} \approx 1.058 \text{ H}$$

3. For  $V = 200 \text{ V}$ ,  $I = 0.625 \text{ A}$ ,  $W = 7 \text{ W}$  and  $f = 50 \text{ Hz}$

(a)

$$X_L = \sqrt{Z^2 - R^2} = \sqrt{320^2 - 17.92^2} \approx \sqrt{102078.8736} \approx 319.49 \Omega$$

(b)

$$L = \frac{X_L}{2\pi f} = \frac{319.49 \Omega}{2\pi \times 50 \text{ Hz}} \approx \frac{319.49}{314.16} \approx 1.017 \text{ H}$$

### 8.0.1 Average Inductance

$$\bar{L} = \frac{L_1 + L_2 + L_3}{3} = \frac{1.585 \text{ H} + 1.058 \text{ H} + 1.017 \text{ H}}{3} = \frac{3.66 \text{ H}}{3} = 1.22 \text{ H}$$

## 9 Result

The average inductance is approximately  $\bar{L} = 1.22 \text{ H}$ .

### 9.1 Discussion

$$R = \frac{W}{I^2}(\Omega)$$

$$Z = \frac{V}{I}(\Omega)$$

$$Z = \sqrt{X^2 - R^2}$$

$$L = \frac{X}{2\pi f}(H)$$